





## Assignment 2

Name: Shasvat Shah



SAP: 60004220126

### Term Test 2

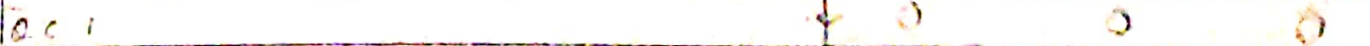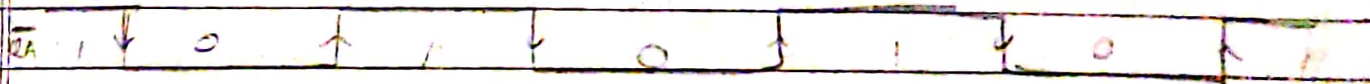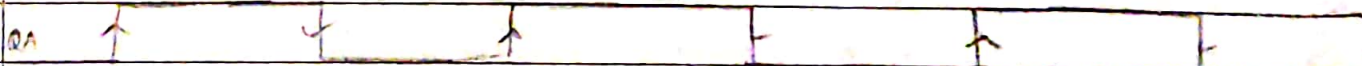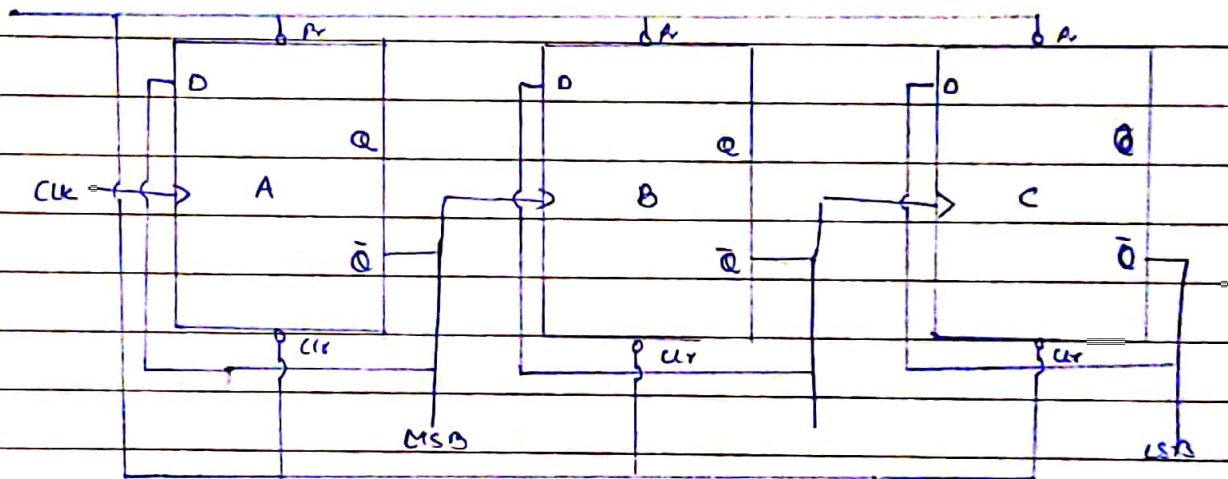1. 3 bit Asynchronous down counter, Rising edge D flip flop.



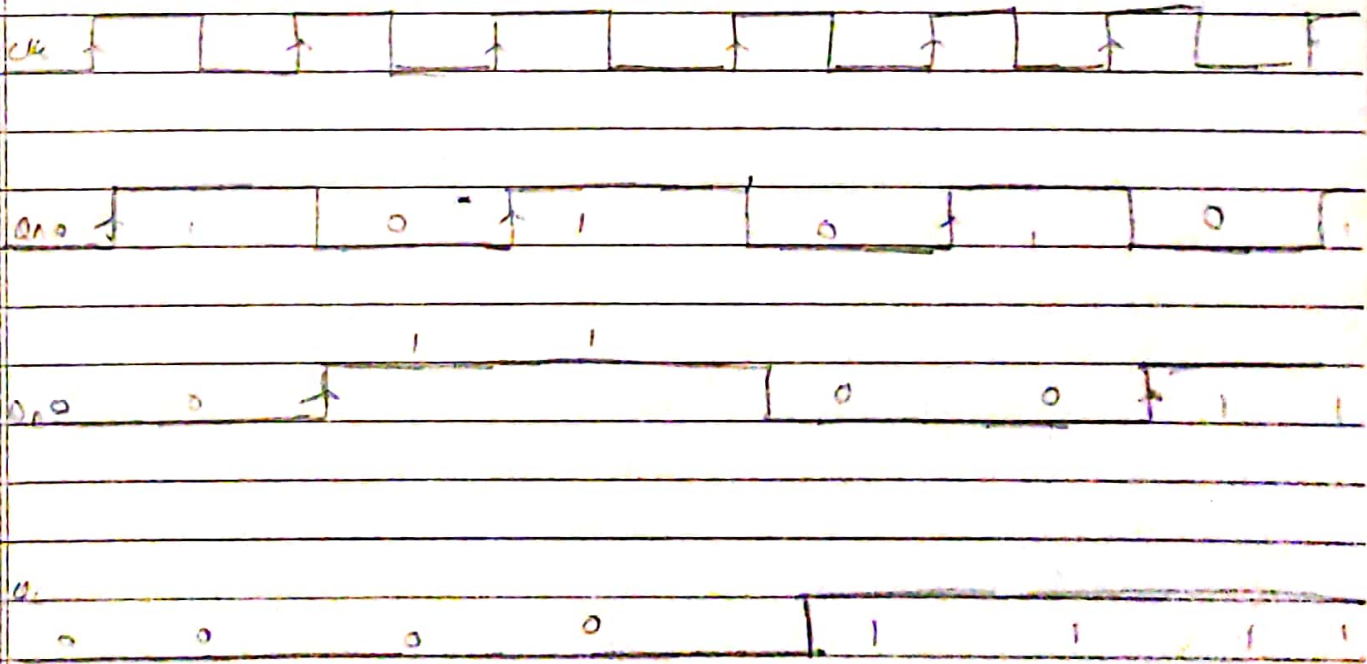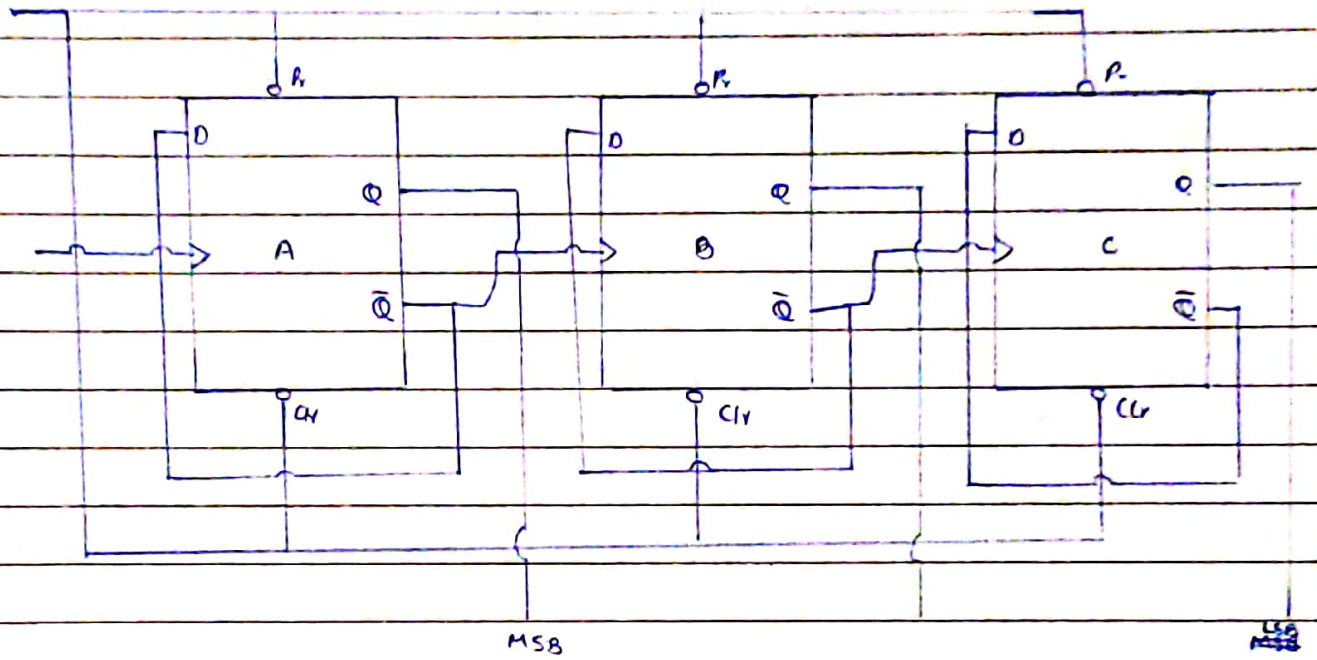Q2 3 bit Asynchronous Up counter. Rising edge. D flipflop.






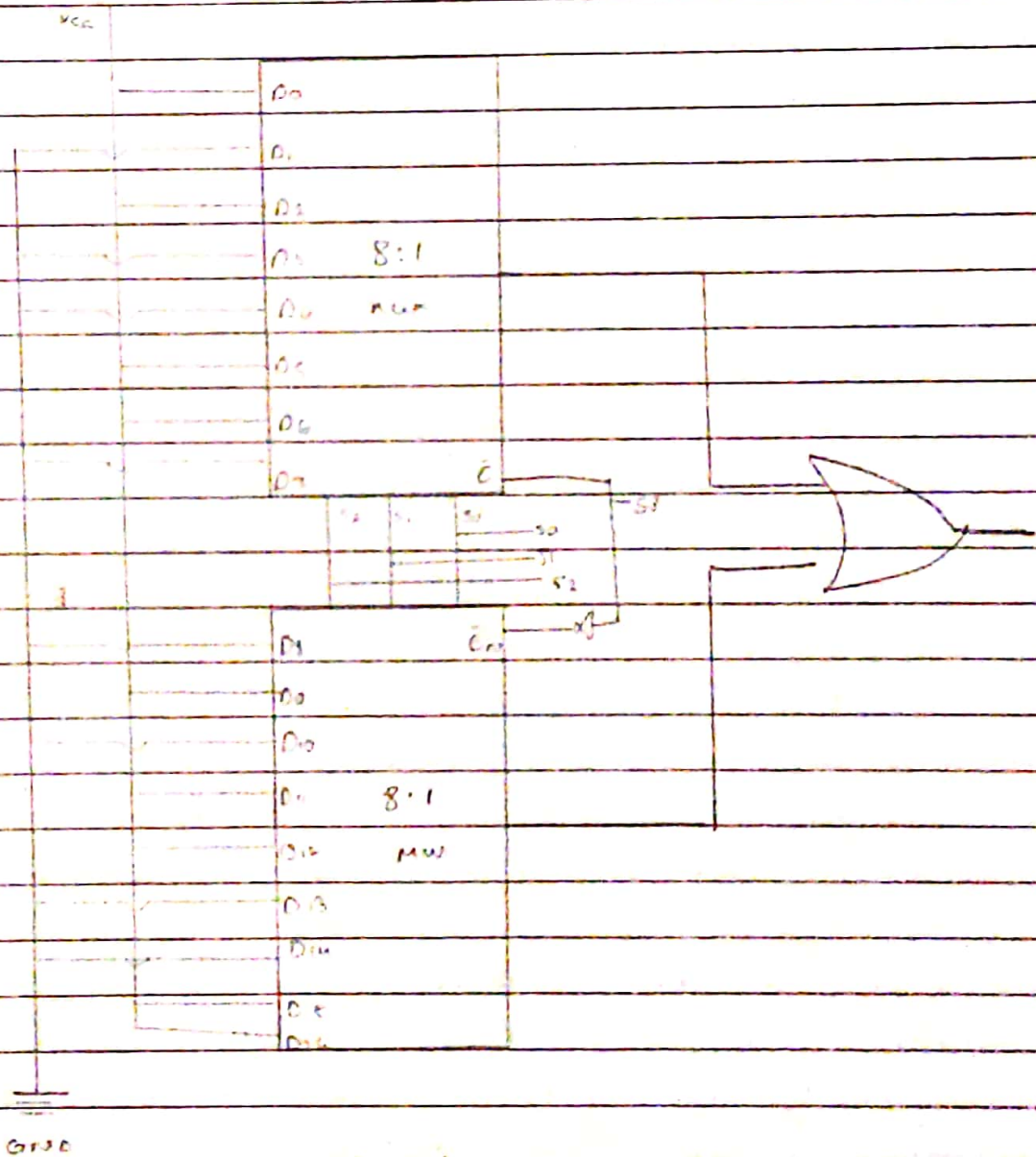2) a. 8


SOP using 8:1 Mux

$$Y = \sum m(0, 2, 3, 6, 9, 11, 12, 15)$$




$$Y = \sum m (0, 2, 3, 6, 9, 11, 12, 15)$$
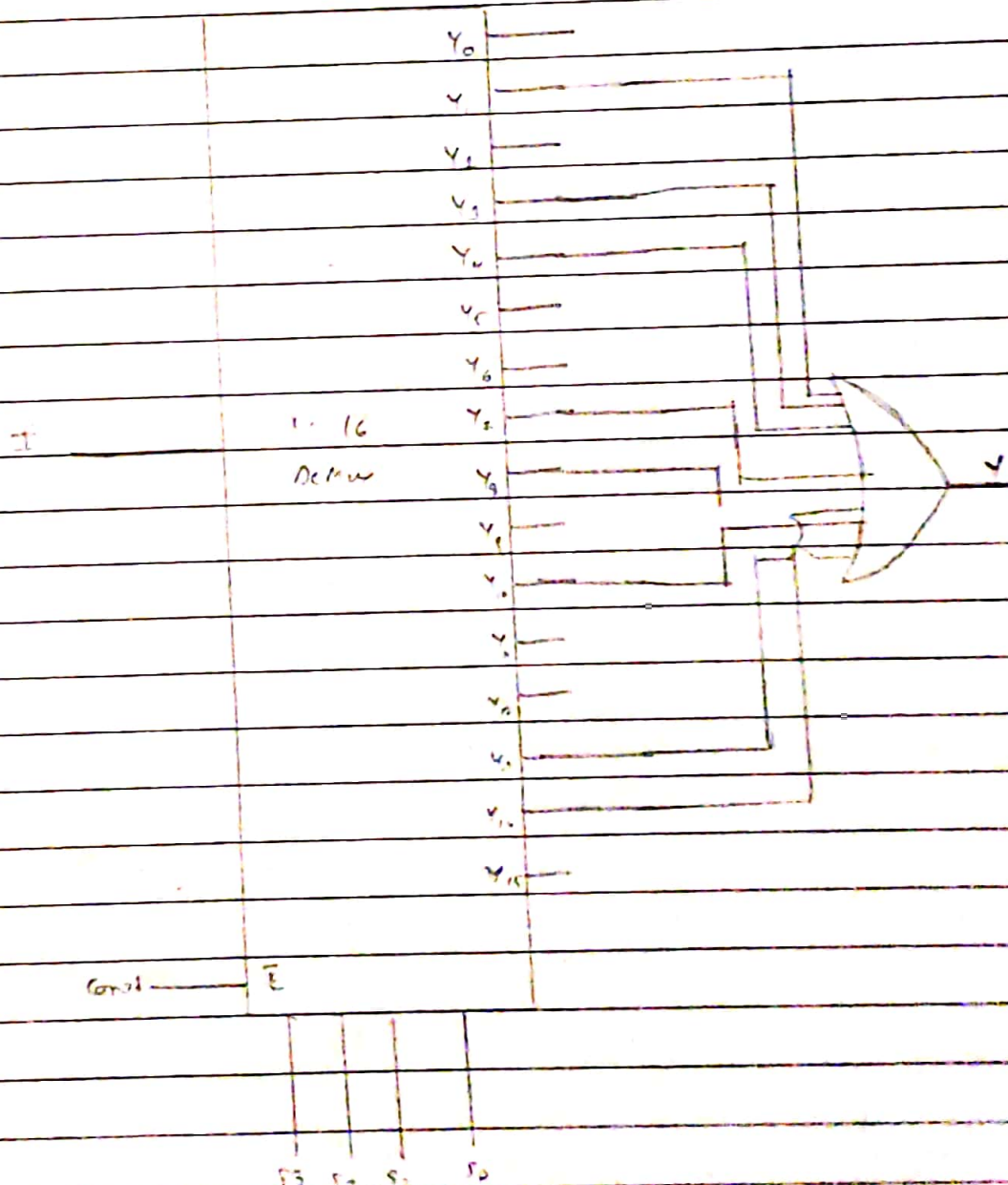
$$Y = \sum m (1, 3, 4, 7, 8, 10, 13, 14)$$






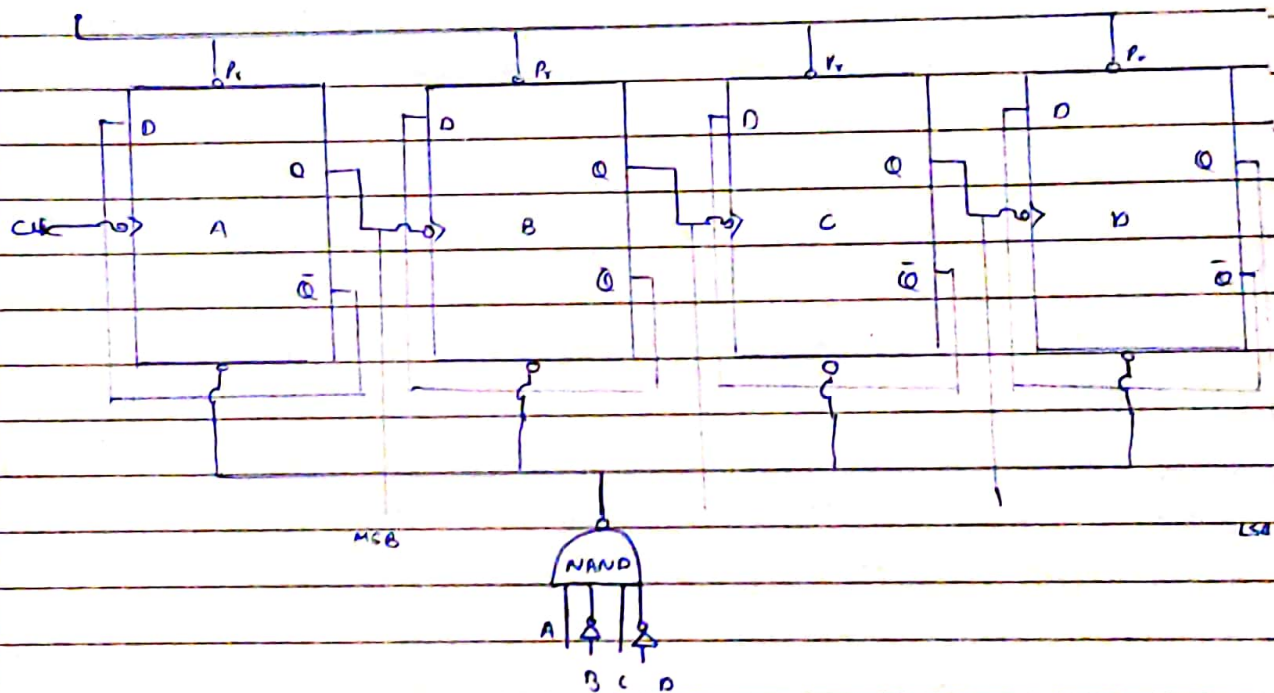3a Mod 10 Asynchronous up counter D flip flop.  
Falling edge.



3b

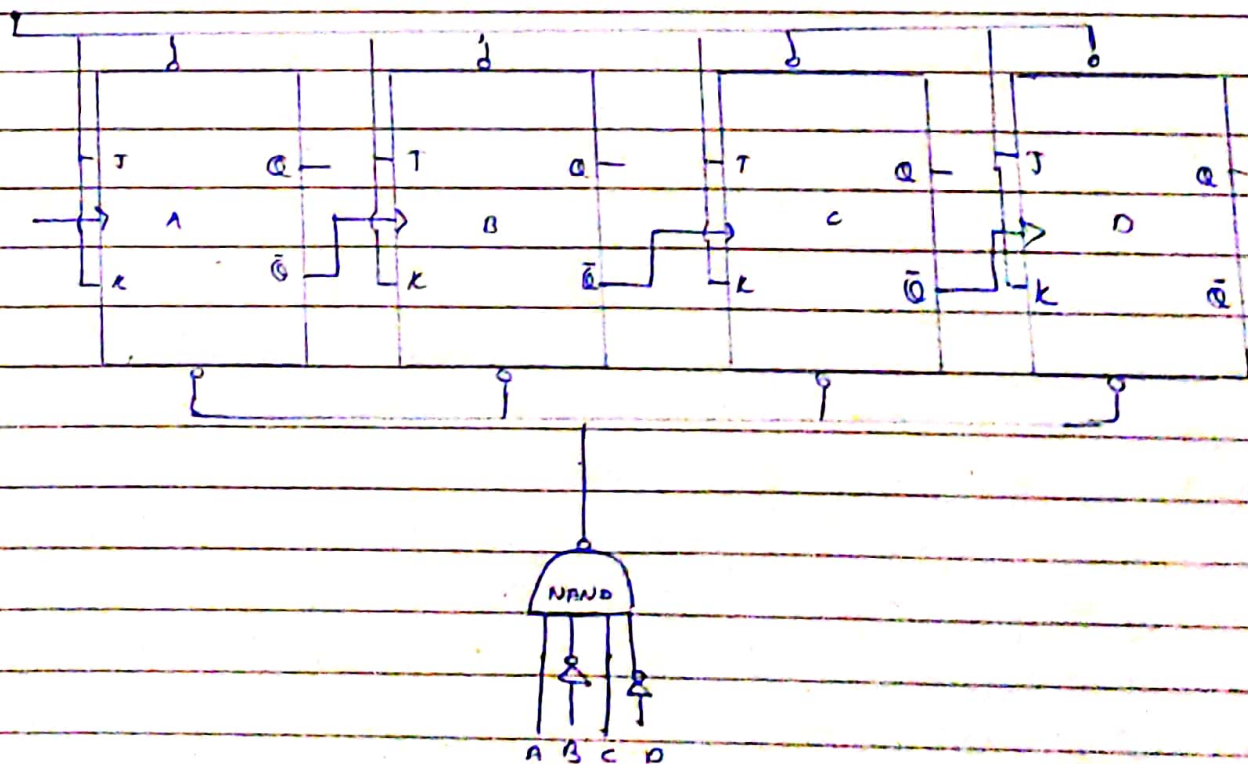

4a) Present and clear are referred as asynchronous inputs in a flip flop.

These are mainly asynchronous.

1) They do not depend on the clock signals whenever they may be.

2) These can be used to set or reset the flip flop.


3) Hence these are very helpful when it comes to mod counters.

4) When the present input is active, the flip flop will become  $Q = 1$  regardless of any clock signal status.

5) When the ~~present~~<sup>clear</sup> input is active, the flip flop will become  $Q = 0$  regardless of the synchronous clock inputs.

6) When multiple flip flops combine together to perform a function, we need to use set or reset to reset them all at once. Hence we use the present and clear inputs.

4b) J.K flip flop.

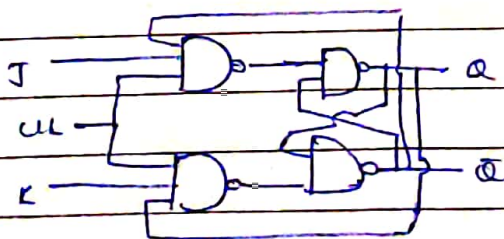

truth table,

CLK	J	K	Q	Q'
0	0	0	Q	Q'
1	0	0	Q	Q'
1	0	1	0	1
1	1	0	1	0
1	1	1	Toggle	



## 5. Seven Segment display configuration.


→ Seven segment display configuration has 7 LEDs, lights and 1 decimal point LED.

Each of the seven segment LED is called a segment.

→ These displays are used in digital clocks, power basic calculators.

→ Segments are named from a to g.

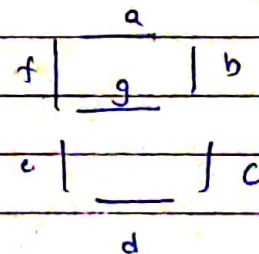→ According to the output required we provide inputs to the seven segment and accordingly LED, light up.



	a	a
	b	b
A <sub>1</sub>	c	c
B <sub>1</sub>	d	d
C <sub>1</sub>	e	e
D <sub>1</sub>	f	f
E <sub>1</sub>	g	g

7 segments

$B_9$	$B_8$	$B_7$	$B_6$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	0	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

5) Explain ways to achieve Binary to Excess 3 code.

→ Excess -3 code can also be represented as XS-3 code.

→ In excess 3 code each digit of decimal number is represented by adding 3 in each decimal digit.

Following steps to convert binary number into excess 3 code.

- 1) Convert the binary number to decimal.
- 2) Add 3 in each digit of decimal number.
- 3) Find binary code of each newly generated number, digit of