
 


11/1/23


Digital Electronics. Term Test II

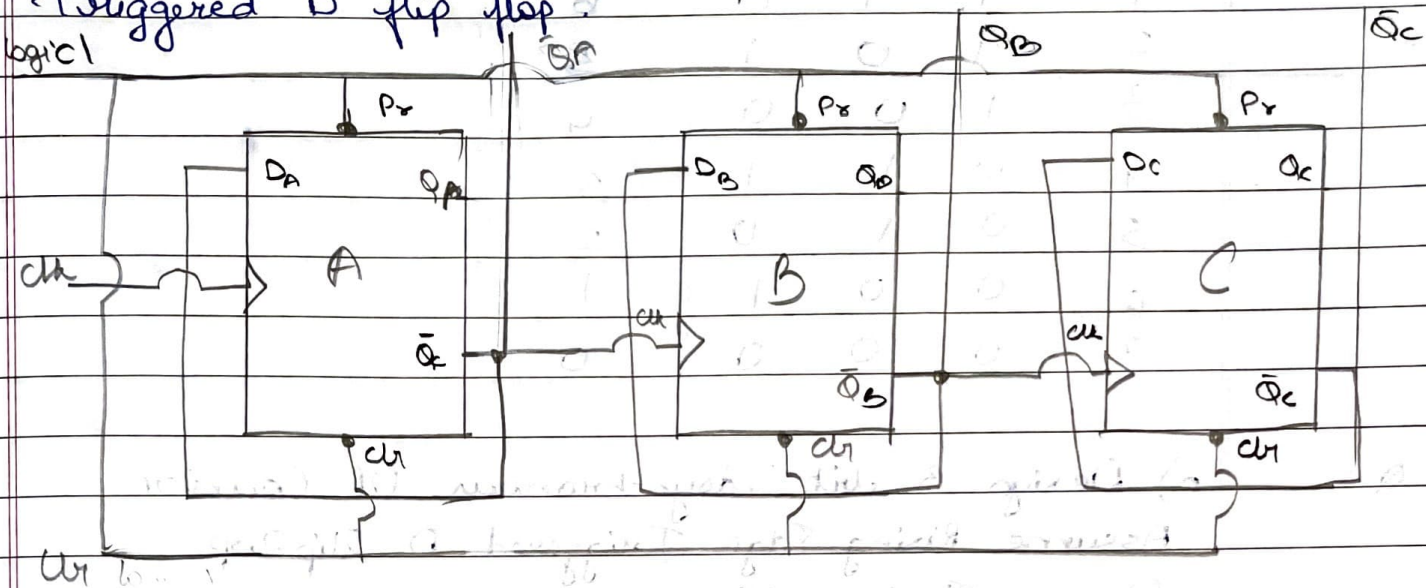
Q.1 a) 3 bit Asynchronous Down Counter, Rising edge Triggered D flip flop



clk	C	B	A	Decimal
0	1	1	1	7
1	1	1	0	6
2	1	0	1	5
3	1	0	0	4
4	0	1	1	3
5	0	1	0	2
6	0	0	1	1
7	0	0	0	0

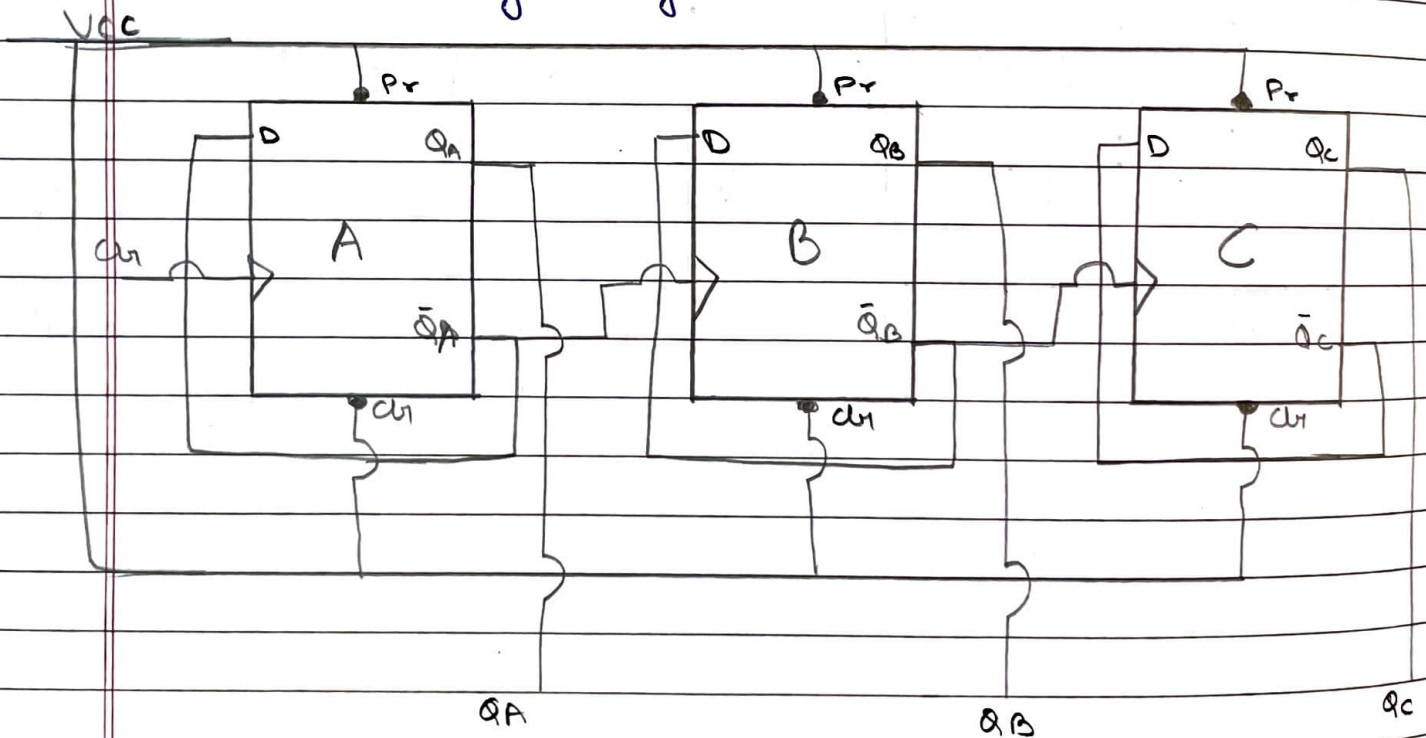Q.1 b) Design 3 bit Asynchronous UP Counter
Assume Rising Edge Triggered D FlipFlop
Draw Timing Diagram




 

CLK	C	B	A	Decimal
0	0	0	0	0
1	0	0	1	1
2	0	1	0	2
3	0	1	1	3
4	1	0	0	4
5	1	0	1	5
6	1	1	0	6
7	1	1	1	7

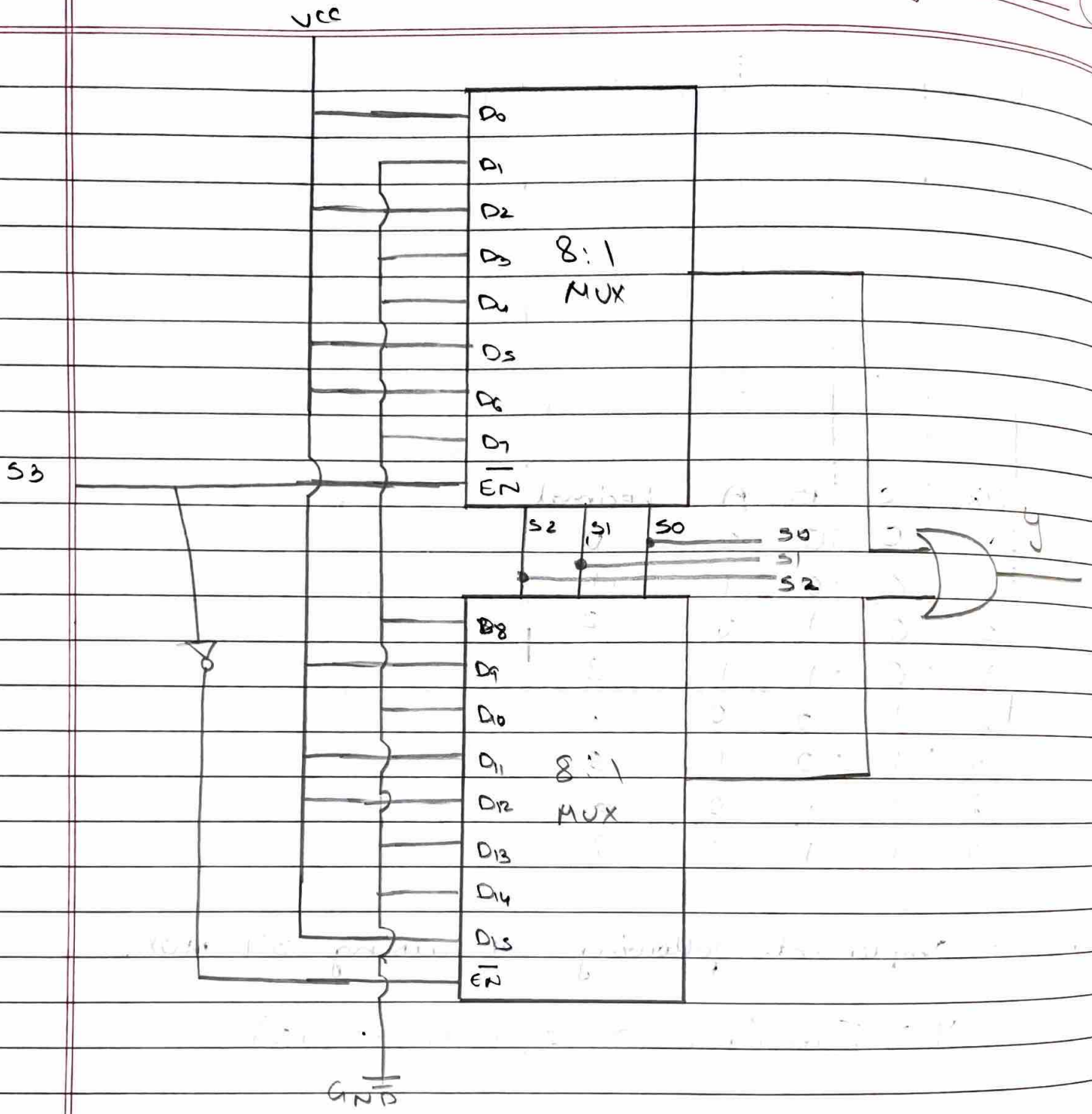Q.2 a) Implement following SOP using 8:1 MUX.


$$Y = \sum m(0, 2, 3, 6, 9, 11, 12, 15)$$



S_3	S_2	S_1	S_0	y
0	0	0	0	1
0	0	0	0 1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1


$$2) \quad y = \frac{\pi}{4} m(0, 2, 5, 6, 9, 11, 12, 15)$$
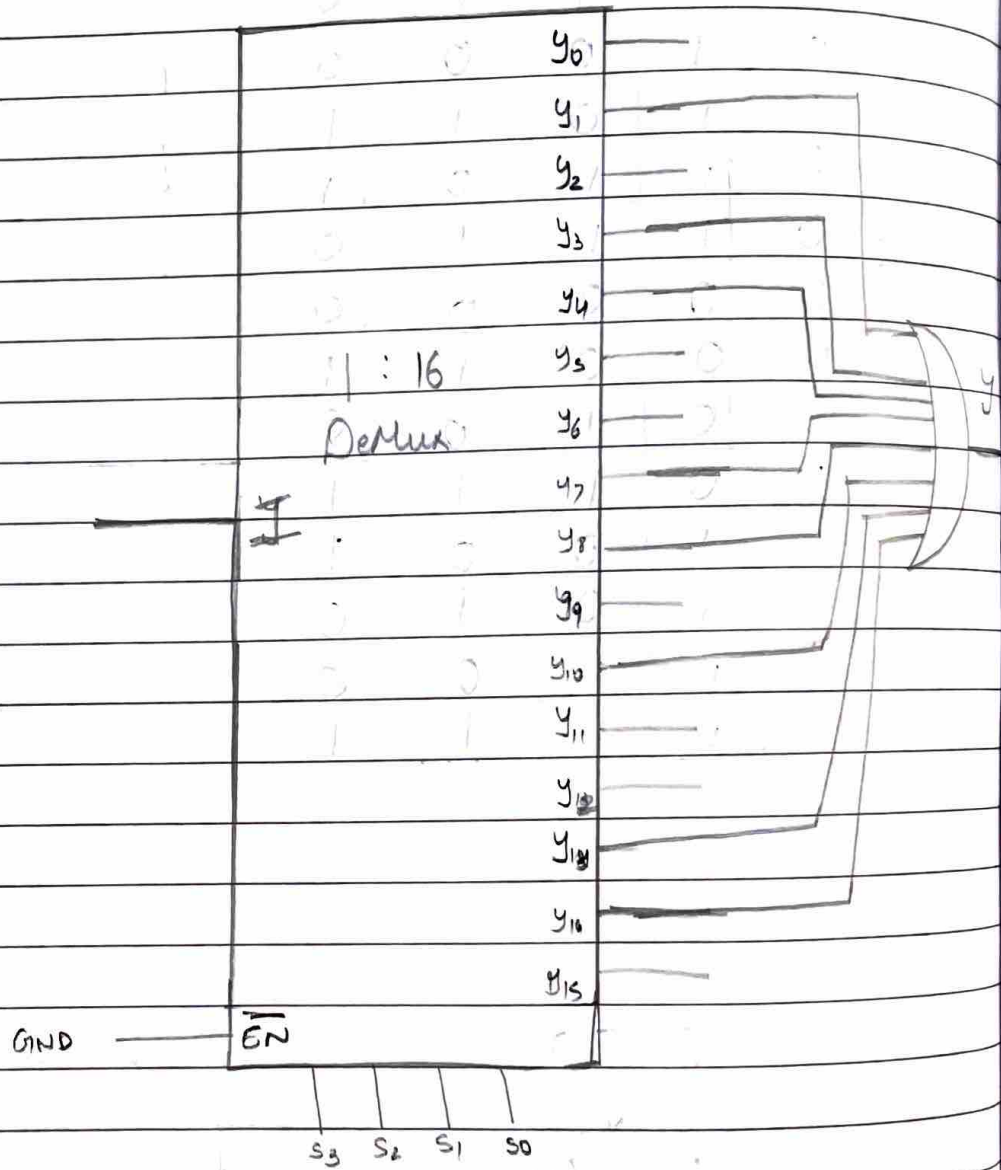
$$y = \sum m(1, 3, 4, 7, 8, 10, 13, 14)$$




S_3	S_2	S_1	S_0	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 Q.3 a) Design MOD 16 to asynchronous up counter using D FF. Assume falling edge triggered. Use full decoding.



 Q. 3 b) Design MOD 10 asynchronous up-counter using J-K flip flop.
assume rising edge triggered. Use full decoding logic.




Q. 4

a) Why are preset and clear referred as asynchronous inputs in a flip flop.

- Preset and clear are called asynchronous inputs because they can set or reset the flip flop regardless of the status of the clock signal.
- When the preset input is activated, the flip flop will be set ($Q=1$, $\bar{Q}=0$) regardless of any of the synchronous inputs or the clock.
- When the clear input is activated, the flip flop will be reset ($Q=0$, $\bar{Q}=1$), regardless of any of the synchronous inputs or the clock.
- Preset and clear inputs find use when multiple

flip-flops are ganged together to perform a function on a multi-bit binary word, and a single line is needed to set or reset them all at once.

 b) Draw and Explain J-k flip flop with truth table.



Truth Table :

clk	J	K	Q_{n+1}	\bar{Q}_{n+1}
0	0	0	Q_n	\bar{Q}_n
1	0	0	Q_n	\bar{Q}_n
1	0	1	0	1
1	1	0	1	0
1	1	1	Toggle (\bar{Q}_n)	

Excitation Table :

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Characteristics Table :


Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0

1	1	0	1
1	1	1	0

Q. 5

 a) Explain Seven Segment display configuration. Also explain BCD to seven segment conversion.

- Seven Segment display configuration has 7 LED lights and 1 (decimal point) LED.
- Each of the seven LED's is called a segment.
- Seven Segment displays are used in digital clocks, basic calculators.
- Segments are named from a. to g.
- According to the output required, we provide inputs to the seven segment and accordingly, the LED's light up.



B ₃ _____	BCD to	a	a
B ₂ _____	7	b	b f g b
B ₁ _____	Segment-	c	c g b
B ₀ _____	d	d	d e c
	e	e	e d
	f	f	f d
	g	g	g

7-Segment

B_3	B_2	B_1	B_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	0	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	0	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1	0	1	1

b) Explain way to achieve Binary to Excess-3 code.

→ • Excess-3 code can also be represented as XS-3 code.

- In excess-3 code each digit of decimal number is represented by adding 3 in each decimal digit.
- Following steps to convert the binary number into Excess-3 code:

- 1) Convert the binary number into decimal.
- 2) Add 3 in each digit of decimal number.
- 3) Find binary code of each digit of the newly generated number.

• Binary to Excess 3

B C D				Excess 3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	0	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0