
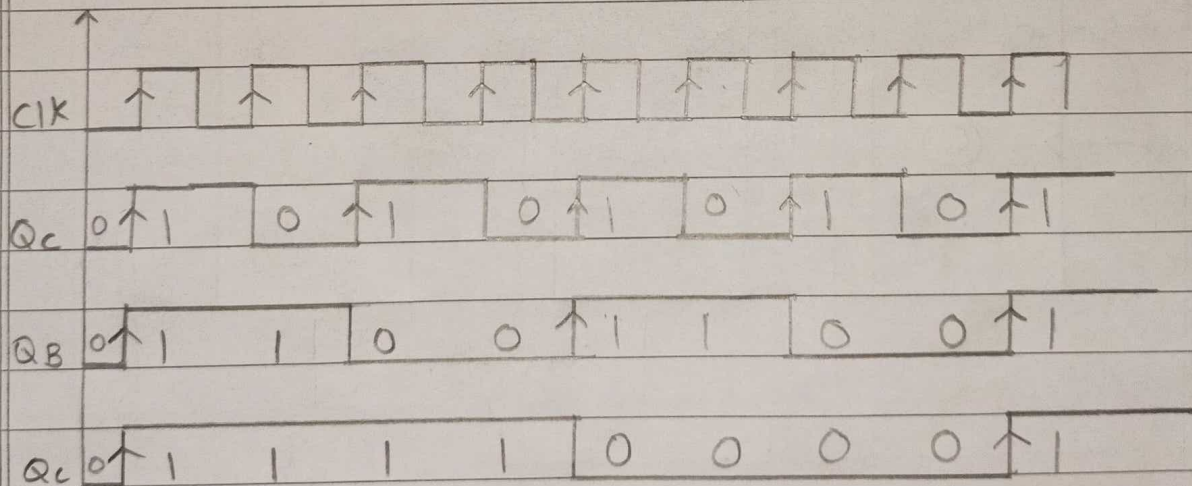


Mihir Vora
60004226115

Digital Electronics TT-2

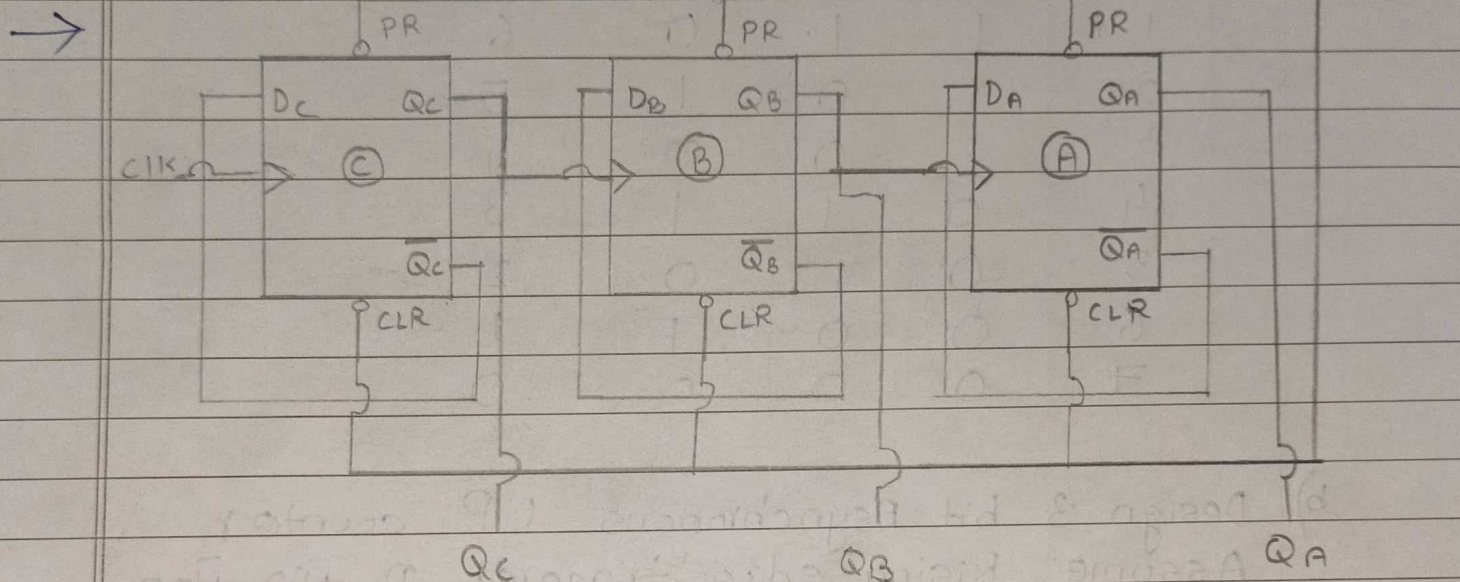
Q.1a) 3 bit Asynchronous down counter using rising edge D FF




Observation Table.

clk	A	B	C	Decimal
0	1	1	1	7
1	1	1	0	6
2	1	0	1	5
3	1	0	0	4
4	0	1	1	3
5	0	1	0	2
6	0	0	1	1
7	0	0	0	0

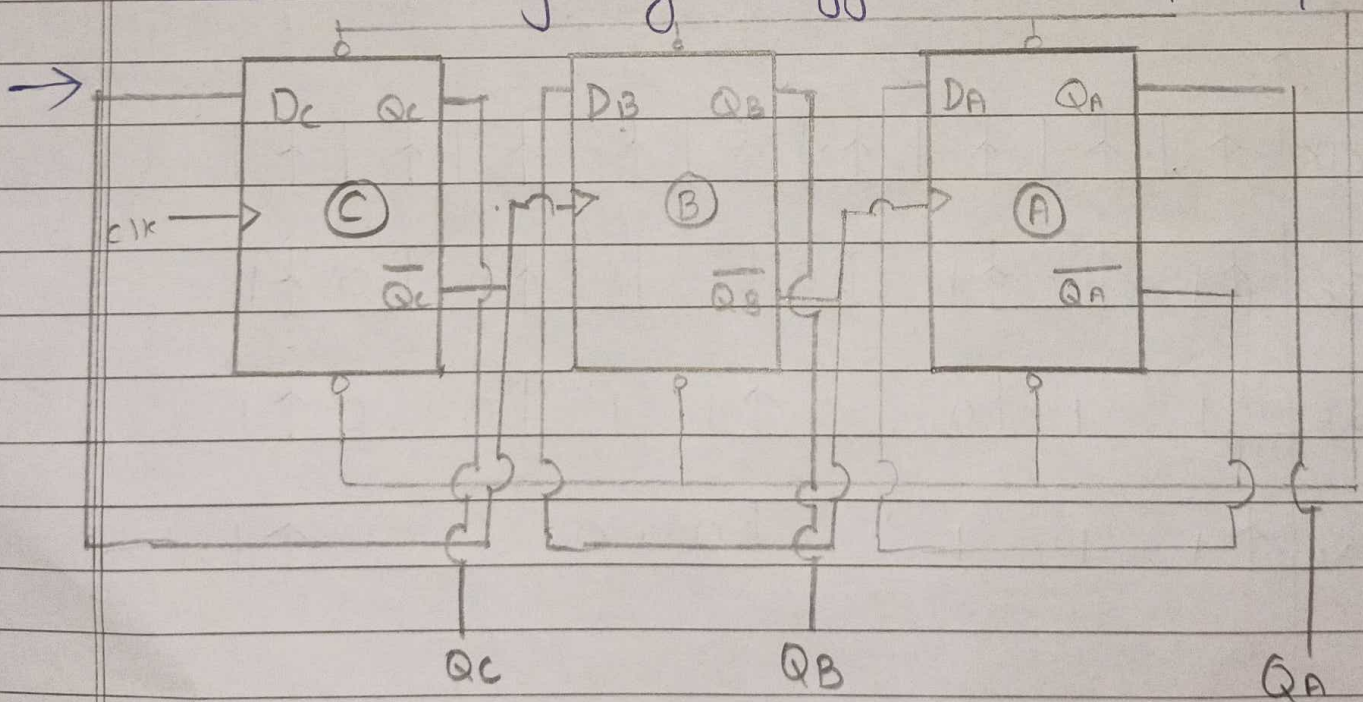
b) Design 3 bit Asynchronous UP counter
Assume Rising edge triggered D flip flop - logic



 


CLK	A	B	C	Decimal
0	0	0	0	0
1	0	0	1	1
2	0	1	0	2
3	0	1	1	3
4	1	0	0	4
5	1	0	1	5
6	1	1	0	6
7	1	1	1	7

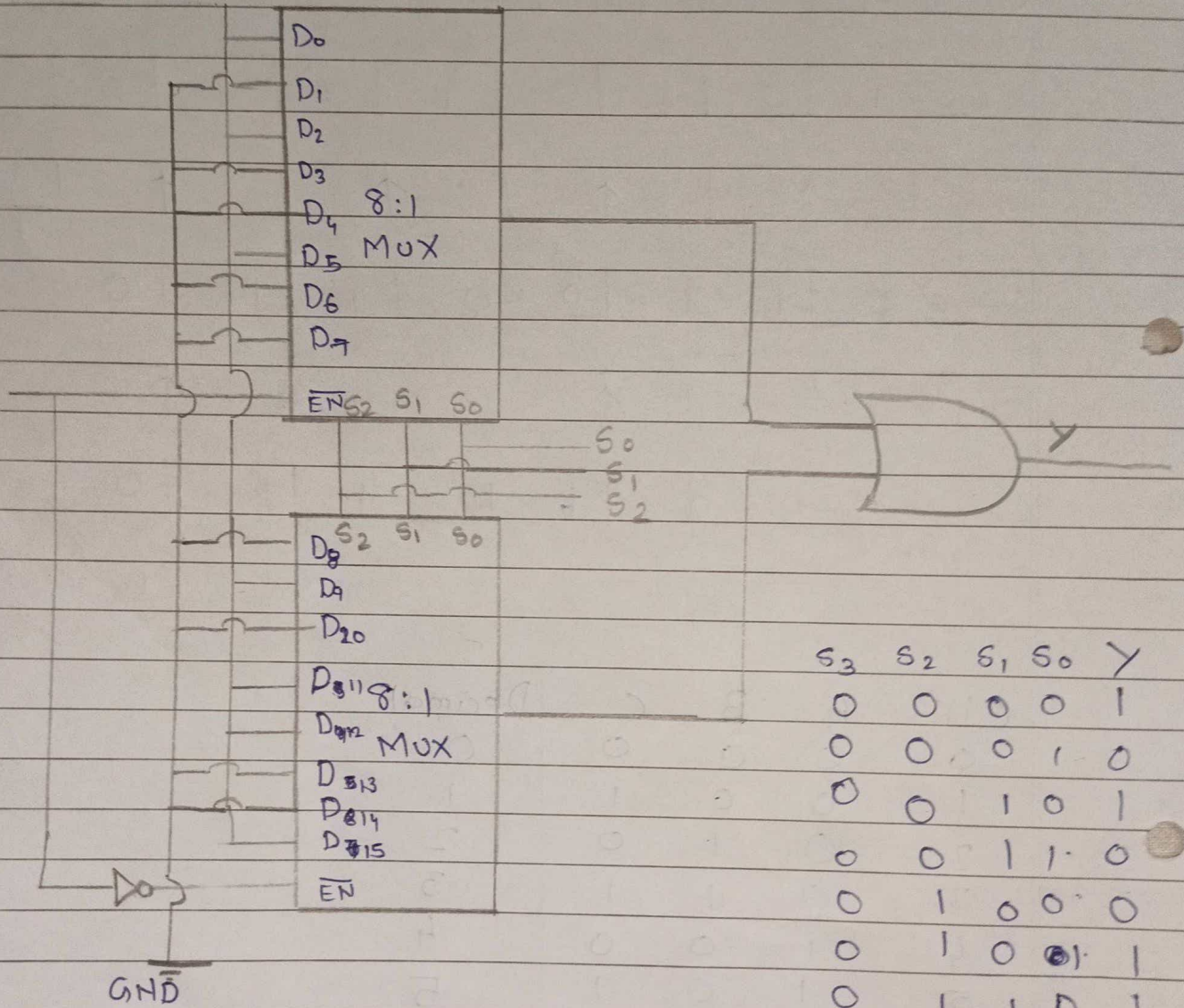Q.2 $Y = \sum_{V_{cc}} m(0, 2, 5, 6, 9, 11, 12, 15)$




S ₃	S ₂	S ₁	S ₀	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

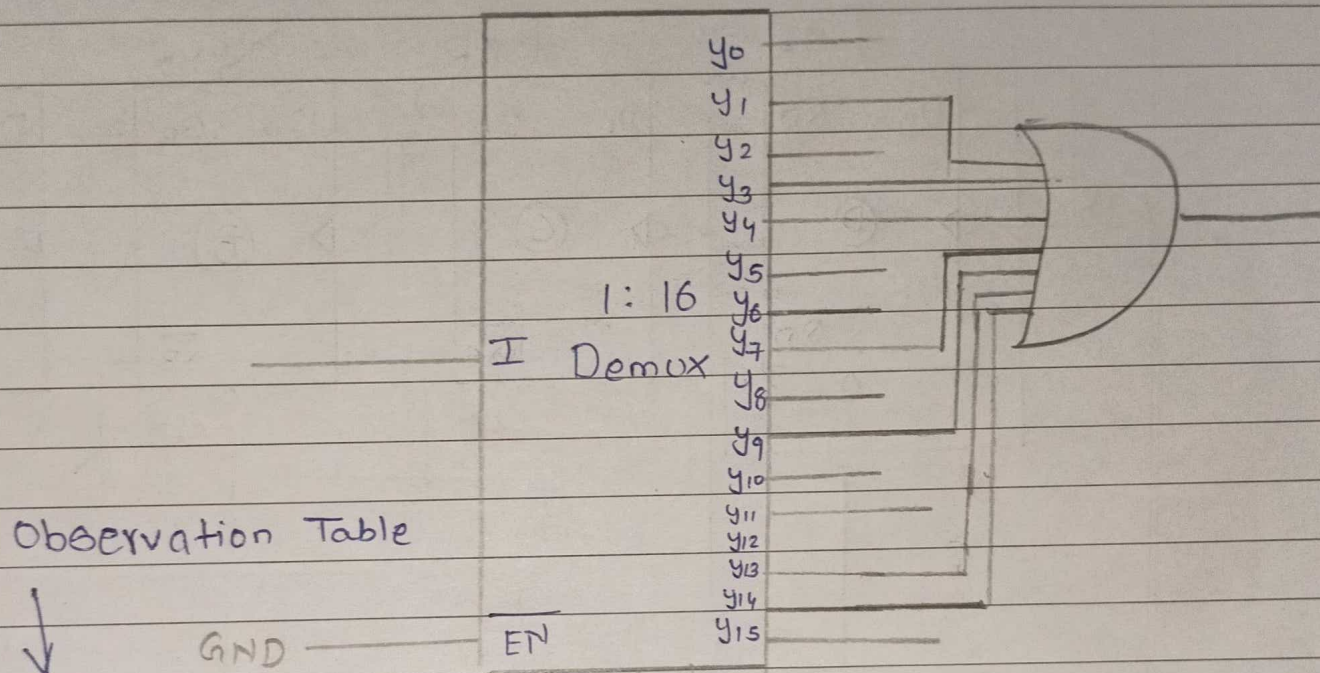b) $Y = \sum \pi m(0, 2, 5, 6, 9, 11, 12, 15)$
 $Y = \sum m(1, 3, 4, 7, 8, 10, 13, 14)$




S_3	S_2	S_1	S_0	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

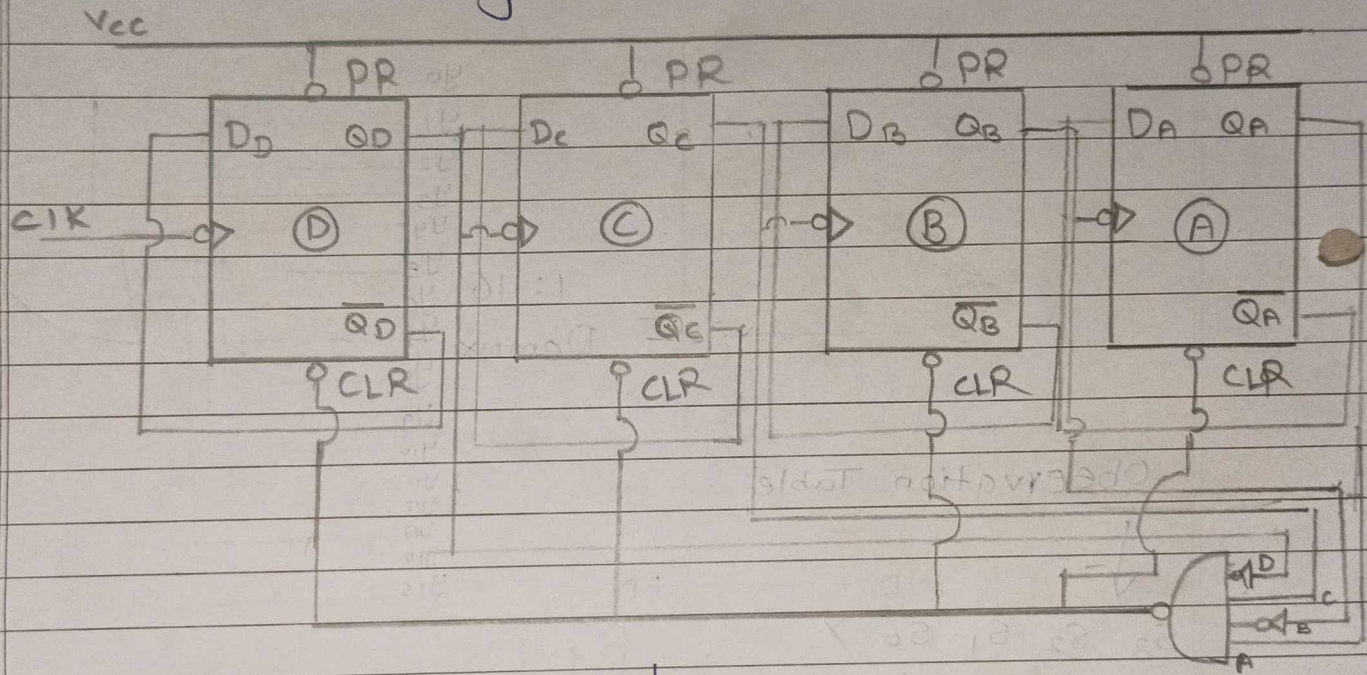Q.3a Design Mod 10 Asynchronous up-counter using D-flip-flop. Assume falling edge triggered. Use Full decoding.



CLK	A	B	C	D	Decimal
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	2
3	0	0	1	1	3
4	0	1	0	0	4
5	0	1	0	1	5
6	0	1	1	0	6
7	0	1	1	1	7
8	1	0	0	0	8
9	1	0	0	1	9
10	0	0	0	0	0

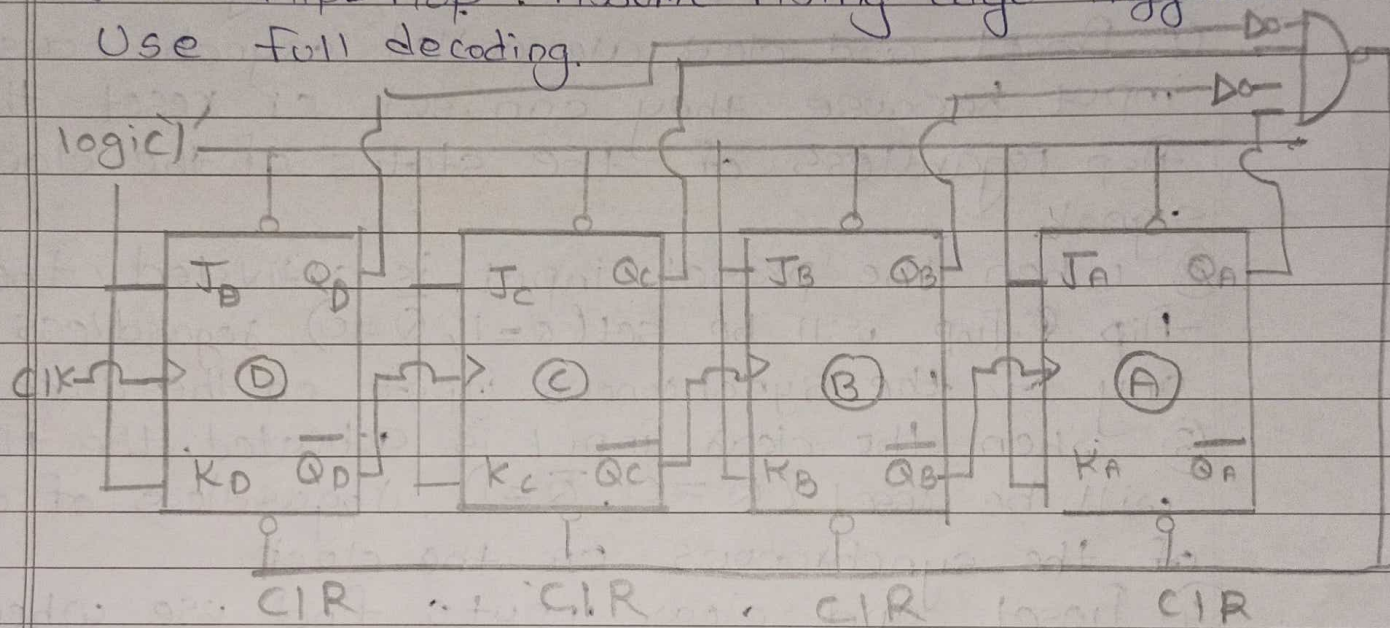Q.3b] Design MOD 10 Asynchronous up-counter using J-K flip-flop. Assume rising edge triggered. Use Full decoding.



Observation Table :

CLK	A	B	C	D	Decimal
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	2
3	0	0	1	1	3
4	0	1	0	0	4
5	0	1	0	1	5
6	0	1	1	0	6
7	0	1	1	1	7
8	1	0	0	0	8
9	1	0	0	1	9
0	0	0	0	0	0

Q.4

a why are preset and clear referred as asynchronous inputs.

→ ① Preset and clear are called asynchronous input because they can set or reset the flip flop regardless of the status of the clock signal.


② When the preset input is activated, the flip flop will be set ($Q=1, \bar{Q}=0$) regardless of any of the synchronous input on the clock.

③ When the clear input is activated, the flip flop will be reset ($Q=0, \bar{Q}=1$), regardless of any of the synchronous on the clock.

④ Preset and clear inputs find use when multiple flip-flops are ganged together to perform a function on a multi-bit binary word, and a single line is needed to set or reset them all at once.

Q.5 Draw and explain J-K flip flop.

b)

 



Truth Table:

clk	J	K	Q_{n+1}	$\overline{Q_{n+1}}$
0	X	X	Q_n	$\overline{Q_n}$
1	0	0	Q_n	$\overline{Q_n}$
1	0	1	0	1
1	1	0	1	0
1	1	1	$\overline{Q_n}$	Q_n

The SR Flip flop has lots of advantages. But it has the following problems. When $S=R=1$ it is an invalid state and is avoided. JK flip flop resolves this problem. The $S=R=1$ is the toggling condition.

 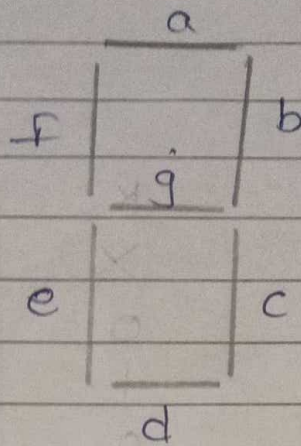Q.5 Explain seven segment display configuration. Also explain BCD to seven segment conversion.

-
- ① Seven segment display configuration has 7 LED lights and 1 (decimal point) LED.
 - ② Each of the seven LED's is called a segment.
 - ③ Seven segment displays are used in digital clocks, basic calculators.
 - ④ Segments are named from a to g.
 - ⑤ According to the output required, we provide inputs to the seven segment and accordingly the LED's light up.



B ₃	B ₂	B ₁	B ₀	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

- b) Explain way to achieve Binary to Excess-3 code
- ① Excess-3 code can also be represented as XS-3 code.
- ② In Excess-3 code each digit of decimal number is represented by adding 3 in each decimal digit.
- ③ Following steps to convert the binary number into Excess-3 code
- 1) Convert the binary number into decimal
 - 2) Add ~~to~~ 3 in each digit of decimal number.
 - 3) Find binary code of each digit of newly generated number.

Binary to Excess-3.

	BCD				Excess-3			
	A	B	C	D	w	x	y	z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

For W

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$W = A + BD + BC$$

For X

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X

$$X = B\bar{C}\bar{D} + \bar{B}D + \bar{B}C$$

For Y

AB \ CD	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	X	X	X	X
10	1	0	X	X

$$Y = \bar{C}\bar{D} + CD$$

For Z

AB \ CD	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X

$$Z = \bar{C}\bar{D} + C\bar{D}$$